

# TI Designs: TIDA-00915

## 200V ACサーボ・ドライブ用、高PWM周波数動作、三相GaNインバータのリファレンス・デザイン



### 概要

TIDA-00915デザインは、200V ACサーボ・モータを2kW<sub>PEAK</sub>で駆動するための三相インバータです。600V、12AのLMG3410窒化ガリウム(GaN)パワー・モジュールが搭載され、FETおよびゲート・ドライバが内蔵されています。GaN FETはシリコンFETよりもはるかに高速にスイッチング可能で、さらにドライバが同じパッケージに統合されているため、寄生インダクタンスが減少し、スイッチング性能が最適化されて電力損失が減少することにより、設計者はヒートシンクのサイズを小さくできます。この容積削減は、小型のサーボ・ドライブやモータ内蔵ドライブに利益があります。インバータは100kHzの高いスイッチング周波数で動作するため、電流リップルが減少し、低インダクタンスのモータとともに使用するときトルク・リップルが改善されます。これによって、位置制御アプリケーションの性能が向上します。


### リソース

TIDA-00915  
LMG3410  
ISO7831  
LM3840  
TLV1117-33  
SN74AHC1G08  
SN74LVC1G11  
AMC1306  
TMDSCNCD28379D

デザイン・フォルダ  
プロダクト・フォルダ  
プロダクト・フォルダ  
プロダクト・フォルダ  
プロダクト・フォルダ  
プロダクト・フォルダ  
プロダクト・フォルダ  
プロダクト・フォルダ  
ツール・フォルダ



E2Eエキスパートに質問

 


### 特長


- 高いPWMスイッチング周波数(最高100kHz)により、低インダクタンスのモータを最小の電流リップルで駆動
- 600V、12AのLMG3410 GaNモジュールと内蔵のFETおよびゲート・ドライバにより、PCBの外形が小さくなり、レイアウトの複雑性が低減
- 非常に高速なスイッチング遷移(25ns未満)で、スイッチ・ノード電圧リンギングがないため、EMIが低減
- 高効率の電力段(100kHz PWMで98%超、24kHz PWMで99%)によりヒート・シンクが小型化
- ゲート低電圧、過電流、過熱に対する保護

### アプリケーション

- モータ内蔵ドライブ
- サーボ・ドライブ
- ロボティクス

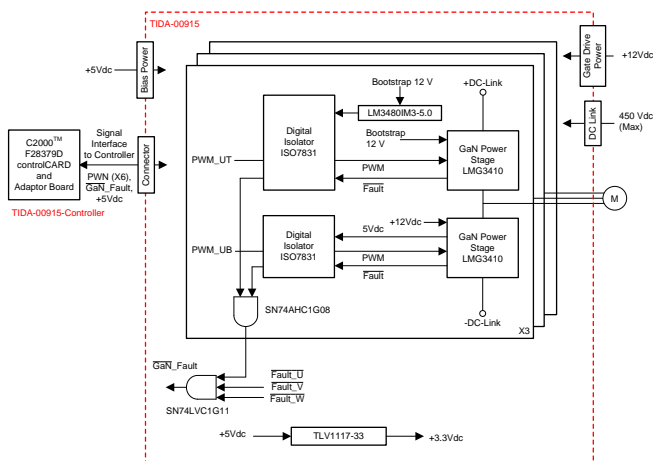

 Copyright © 2017, Texas Instruments Incorporated





使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、[www.ti.com](http://www.ti.com)で閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

## 1 System Description

High-voltage brushless motors with low inductance and high speed are used in precision applications like servo drives, CNC machines, and industrial robotics. There is a need for driving low-inductance motors using a three-phase inverter at a high switching frequency to reduce the torque ripple in the motor and minimize the losses in the motor.

The phase current ripple is inversely proportional to the switching frequency of the pulse width modulation (PWM). The phase current ripple contributes to motor losses, which reduce the efficiency of the motor and increase the temperature of the motor. These losses are especially present in motor-integrated power electronics and multi-axis drives used in service robots, where any additional motor losses limit the maximum power of the device over the rated operating temperature range.

For precision servo drives, which require high position accuracy, a torque ripple can have a negative impact on static position accuracy. The motor phase-current ripple must be reduced to reduce the torque ripple for a given motor, which can be achieved by increasing the inverter PWM switching frequency.

However, inverters based on IGBTs cannot increase the switching frequency above 40 kHz due to large switching losses. The switching losses necessitates to use a larger heat sink with an IGBT. A larger heat sink increases the system cost, weight, and space. The solution to this problem is to use gallium nitride GaN FETs, which can operate with much lower power dissipation. 表 1 shows the advantage GaN-FETs have over Si-FETs.

表 1. Comparison of Silicon MOSFET and TI's GaN FET (HEMT)

PARAMETER	Si-FET	TI's GaN (HEMT)	COMMENTS
Device structure	Vertical	Lateral	The TI GaN FET and driver are in the same package, which reduces parasitic inductances and optimizes switching performance
$R_{DS\_ON}$ , area metric	$> 10 \text{ m}\Omega\text{-cm}^2$	Lateral 5 to 8 $\text{m}\Omega\text{-cm}^2$	Lower conduction losses
Gate charge $Q_G$	$\approx 4 \text{ nC-}\Omega$	$\approx 1 \text{ to } 1.5 \text{ nC-}\Omega$	Reduces gate driver losses and enables faster switching, lower switching losses, and lower dead band distortions
Reverse recovery $Q_{RR}$	$\approx 2 \text{ to } 15 \text{ }\mu\text{C-}\Omega$	—	Zero reverse-recovery enables efficient half-bridge inverters and reduces or eliminates ringing in hard switching

GaN transistors can switch much faster than silicon MOSFETs, which allows the potential to achieve lower switching losses. However, at high slew rates, certain package types can limit GaN FET switching performance. Integrating the GaN FET and driver in the same package reduces parasitic inductances and optimizes switching performance. The faster switching is achieved with little or no turnon or turnoff ringing, which reduces the electromagnetic interferences. For more details, see the GaN white paper page (SLYY071).

The low-power dissipation benefits servo and embedded drives. In servo drives, the low-power dissipation results in a small form factor. In embedded drives, the drive electronics is enclosed inside the motor hub, and the inverter uses the motor frame as the heat sink. Here the inverter has to operate at high ambient temperatures with little cooling. The low-power dissipation allows the embedded drive inverter to deliver more power for the same operating temperature.

The TIDA-00915 is a three-phase inverter for driving 200-V AC servo motors with 2 kW<sub>PEAK</sub>. It features a 600-V and 12-A LMG3410 GaN power module with an integrated FET and gate driver. The inverter is able to operate at a high switching frequency of 100 kHz, which reduces the current ripple and improves torque ripple when used with low-inductance motors. The TIDA-00915 has the three-phase inverter with the required isolation, DC-link voltage sensing, and inline current sensing. The TIDA-00915 board supports interface to a C2000™ F28379D control card through an adaptor card. The adaptor card is designated as TIDA-00915-Controller.

## 1.1 Key System Specifications

表 2. Key System Specifications

PARAMETER	SPECIFICATION
DC link voltage	300 V (200 to 450 V)
Output voltage	Three-phase 220-V AC
Current	4.5 A <sub>RMS</sub> continuous
Nominal output power	1.5 kW
Peak output power	2 kW
Slew rate	20 kV/μs
PWM switching frequency	100 kHz
PWM dead-band	50 ns
Efficiency	99% at 24 kHz, 2-kW output power 98% at 100 kHz, 2-kW output power
Protection	UVLO protection on gate drive power supply (9.3 V) Overcurrent protection (24 A) Overtemperature protection (160°C)
Feedback	Three inline isolated current sensing DC-Link Voltage sensing
Host controller interface	3.3-V I/Os with: <ul style="list-style-type: none"> <li>6× PWM signals for three phase inverter</li> <li>4× delta-sigma modulated feedback signals</li> </ul>
PCB form factor	180 mm × 82 mm 4 layers 1.6-mm thickness



The low-voltage side is powered from an external 5-V input. A TLV1117-33 LDO is used to generate a 3.3-V rail from this 5-V input for powering the MCU side of the digital isolator. An external 12-V gate drive power supply is used, which has to be isolated from the 5-V input given on the low-voltage side. The 12-V gate drive power supply biases the three low-voltage GaN modules. A three-bootstrap 12-V rail is derived from the gate drive power supply for the three high-side GaN modules. The GaN module generates 5-V and –12-V rails, which are used internally. This 5-V rail is also used to bias the three bottom digital isolators. The high-voltage side of the top digital isolator is powered from the LM3480 5-V LDO.


The inverter power stage interfaces to the C2000 control card. There is an adaptor board (TIDA-00915-Controller) on which the control card is inserted. The adaptor board interfaces the TIDA-00915 through a ribbon cable. The C2000 control card implements a simple space vector modulated PWM to generate a rotating voltage vector where the voltage vectors frequency and magnitude can be controlled. The firmware is based on the [controlSUITE™ library](#).

## 2.2 Highlighted Products
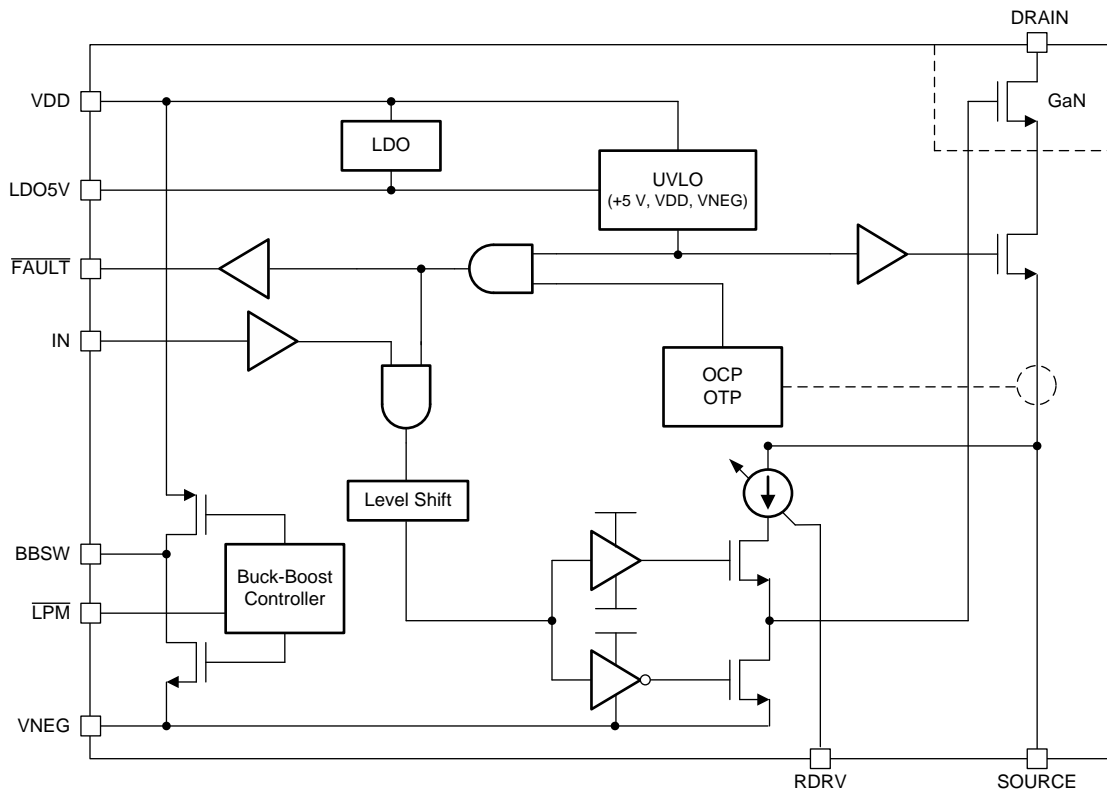
### 2.2.1 LMG3410

The LMG3410 Single-Channel GaN Power Stage contains a 70-mΩ, 600-V GaN power transistor and specialized driver in an 8-mm by 8-mm QFN package. The Direct Drive architecture is used to create a normally-off device while providing the native switching performance of the GaN power transistor. When the LMG3410 is unpowered, integrated low-voltage silicon MOSFET turns the GaN device off at its source. In normal operation, the low-voltage silicon MOSFET is held on continuously while the GaN device is gated directly from an internally generated negative voltage supply.

The integrated driver provides additional protection and convenience features. Fast overcurrent, overtemperature, and UVLO protections help create a fail-safe system; the device's status is indicated by the FAULT output. An internal 5-V low-dropout regulator (LDO) can provide up to 5 mA to supply external signal isolators. Finally, externally-adjustable slew rate and a low-inductance QFN package minimize switching loss, drain ringing, and electrical noise generation.



Copyright © 2017, Texas Instruments Incorporated

図 2. Functional Block Diagram of LMG3410

## 2.2.2 ISO7831

The ISO7831x device is a high-performance, three-channel digital isolator. This device has isolation certifications according to VDE, CSA, TUV, and CQC. The ISO7831x device also incorporates advanced circuit techniques to maximize the CMTI performance with an industry leading CMTI of  $\pm 100\text{-kV}/\mu\text{s}$  minimum. The isolator provides high EMI and low emissions at low power consumption, while isolating CMOS or LVCMOS digital I/Os.

Each isolation channel has a logic input and output buffer separated by silicon dioxide ( $\text{SiO}_2$ ) insulation barrier. The ISO7831x device has two forward and one reverse-direction channels. If the input power or signal is lost, the default output is high for the ISO7831 device and low for the ISO7831F device.

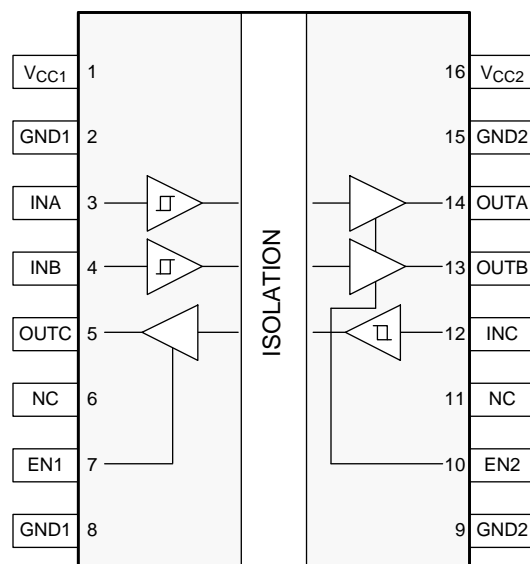


図 3. Functional Block Diagram of ISO7831

### 2.2.3 LM3480

The LM3480 is an integrated linear voltage regulator. It features operation from an input as high as 30 V and an ensured maximum dropout of 1.2 V at the full 100-mA load. Standard packaging for the LM3480 is the three-lead SOT-23 package.

The 5-V, 12-V, and 15-V members of the LM3480 series are intended as tiny alternatives to industry standard LM78Lxx series and similar devices. The 1.2-V quasi-low dropout of LM3480 series devices makes them a nice fit in many applications where the 2- to 2.5-V dropout of LM78Lxx series devices precludes their (LM78Lxx series devices) use. The LM3480 series also features a 3.3-V member. The SOT-23 packaging and quasi-low dropout features of the LM3480 series converge in this device to provide a very nice, very tiny bias supply.

### 2.2.4 TLV1117

The TLV1117 device is a positive low-dropout voltage regulator designed to provide up to 800 mA of output current. The device is available in 1.5-V, 1.8-V, 2.5-V, 3.3-V, 5-V, and adjustable-output voltage options. All internal circuitry is designed to operate down to 1-V input-to-output differential. Dropout voltage is specified at a maximum of 1.3 V at 800 mA, decreasing at lower load currents. The TLV1117 device is designed to be stable with tantalum and aluminum electrolytic output capacitors having an ESR between 0.2 and 10  $\Omega$ . Unlike pnp-type regulators, in which up to 10% of the output current is wasted as quiescent current, the quiescent current of the TLV1117 device flows into the load, increasing efficiency.

### 2.2.5 AMC1306

The AMC1306 is a precision, delta-sigma ( $\Delta\Sigma$ ) modulator with the output separated from the input circuitry by a capacitive double isolation barrier that is highly resistant to magnetic interference. This barrier is certified to the DIN V VDE V 0884-10 and cUL1577 standards. Used in conjunction with isolated power supplies, the device prevents noise currents on a high common-mode voltage line from entering the local system ground and interfering with or damaging low-voltage circuitry.



The input of the AMC1306 is optimized for direct connection to shunt resistors or other low-voltage level signal sources. The unique low input voltage range of the  $\pm 50$ -mV device allows significant reduction of the power dissipation through the shunt while supporting excellent AC and DC performance. The output bit stream of the AMC1306 is Manchester coded (AMC1306Ex) or un-coded (AMC1306Mx), depending on the derivate. By using an appropriate digital filter (that is, as integrated on the TMS320F2807x or TMS320F2837x families) to decimate the bit stream, the device can achieve 16 bits of resolution with a dynamic range of 81 dB (13.2 ENOB) at a data rate of 78 kSPS. On the high-side, the modulator is supplied by a 3.3- or 5-V power supply (AVDD). The isolated digital interface operates from a 3.0-V, 3.3-V, or 5-V power supply (DVDD). The AMC1306 provides a very high CMTI performance of 100 kV/ $\mu$ s, required in high-switching environments like GaN inverter to suppress data corruption.

## 2.3 System Design Theory

### 2.3.1 Three Phase GaN Inverter Power Stage

The three-phase GaN inverter is realized with six LMG3410 GaN modules. [Figure 4](#) shows the DC-link input and the three-phase output of the inverter section. The power stage consist of three identical half bridges; one of the half-bridge is shown in [Figure 5](#).

#### 2.3.1.1 Bypass and Bulk Capacitors

Two film capacitor (C50 and C51 in [Figure 4](#)) of 3  $\mu$ F each is used on the DC-link input to suppress any transient voltage spikes due to switching. Each half bridge also has additional local capacitors (C81 to C86 in [Figure 5](#)) of 0.14  $\mu$ F. The bulk capacitors, which are usually kept after the AC-to-DC rectification in the end application, are not placed on the board. The end system using the GaN inverter should have this to reduce voltage variation when operating from AC mains. However, for lab testing, this is inconsequential as the DC-link is powered from a well-regulated high voltage power supply. A bleeder resistors consisting of three series resistors of 100 k $\Omega$  are placed between the DC-link capacitors. This is done to discharge the capacitor when the turned DC-link power is switched off.


#### 2.3.1.2 Inverter Power Capability

The LMG3410 can support maximum peak current of  $\pm 12$  A<sub>PEAK</sub>, which corresponds to an RMS current of 8.4 A<sub>RMS</sub>. The 8.4-A<sub>RMS</sub> value should not be exceeded during operation. The 8.4 A<sub>RMS</sub> is a momentary maximum current rating for the TIDA-00915. The continuous current is determined by the thermal design. The board should be able to deliver 4.5 A<sub>RMS</sub> (I<sub>RMS</sub>) continuously at full speed, which is at 200 V<sub>AC</sub> (V<sub>RMS</sub>) and at the unity power factor. The corresponding power is given by [Equation 1](#), which is the output power for a balanced three phase output.

$$P_{OUT} = \sqrt{3} \times V_{RMS} \times I_{RMS} \times PF \quad (1)$$

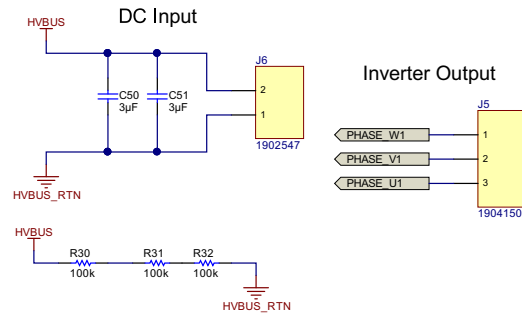
The rated output power is calculated as  $P_{OUT} = \sqrt{3} \times 200 \text{ V} \times 4.5 \text{ A} \times 1 = 1558 \text{ W}$ .





Copyright © 2017, Texas Instruments Incorporated

図 4. DC-Link Input and Three-Phase Output Schematic

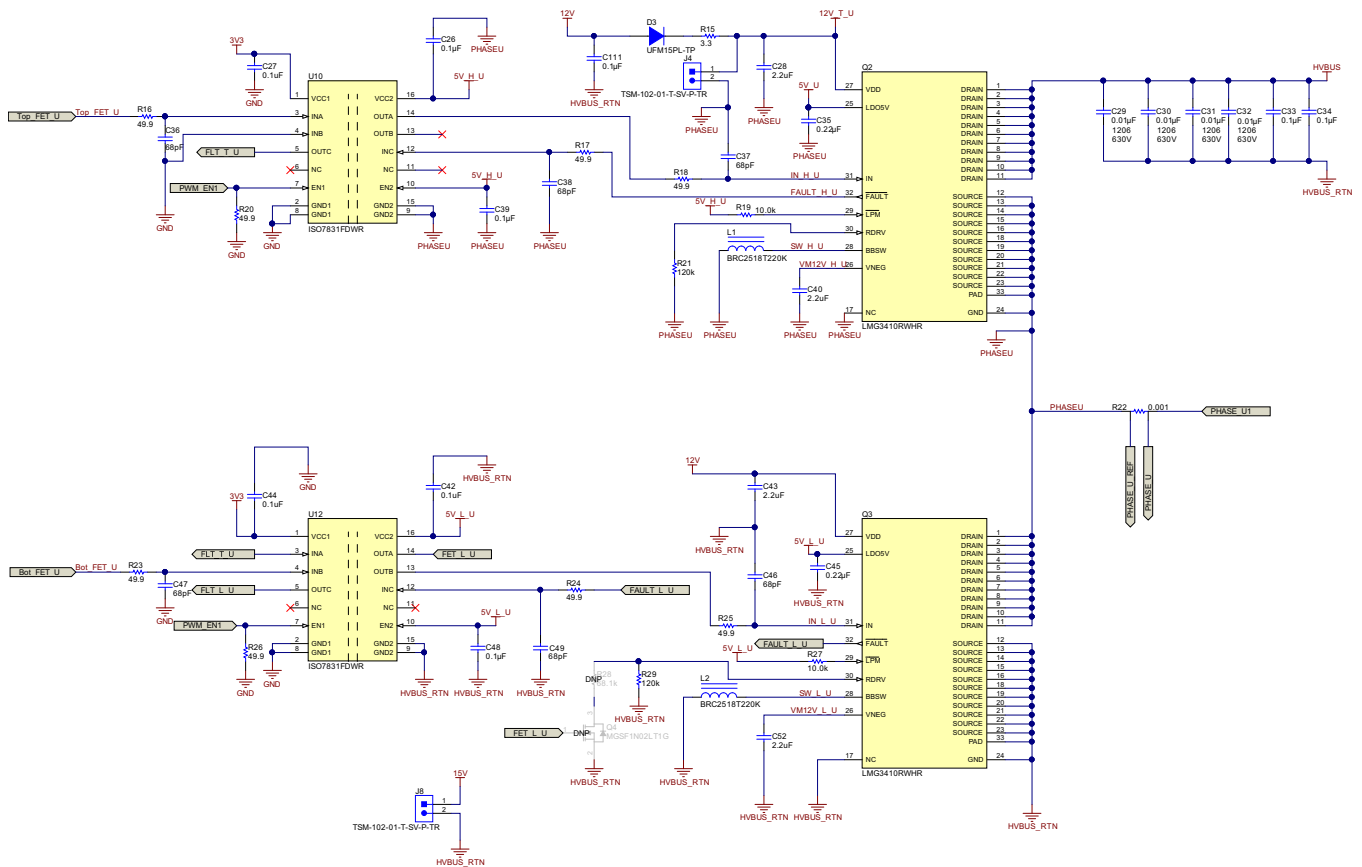

Copyright © 2017, Texas Instruments Incorporated

図 5. Half Bridge of GaN Inverter Schematic

### 2.3.1.3 Power Stage Half Bridge

The power stage consist of three identical half bridges; one of the half-bridge is shown in 図 5. Each GaN module generates 5 V from an internal LDO, which is used internally and also to power the high-voltage side of digital isolator for the bottom GaN module. C87 and C97 in 図 6 are the bulk capacitors for this 5-V LDO. The high-voltage side of the top digital isolator is biased by the 5-V LDO connected to the 15-V bootstrap power supplies. The GaN module also generates a negative 12-V power supply rail for the gate drive using an internal switching regulator, L5 and C92, and L6 and C102 are the passive components for this regulator. The RDRV pin of the GaN module is used to set the switching transient, a 120-k $\Omega$  value set the dV/dt to 20 V/ns.


Isolation is required between the GaN module, which is on the high-voltage side, and the controller generating the PWM, which is on the low-voltage side. The PCB employs two separated ground planes to achieve this galvanic isolation. The digital isolator is chosen to support a very high CMTI of 100 kV/ $\mu$ s. Each digital isolator is used to give a PWM input to the GaN module and also to take  $\overline{\text{FAULT}}$  feedback from the GaN module to the low-voltage side.

### 2.3.1.4 Gate Drive Power Supply

The low-side gate drivers for all three channels are powered using 15 V, which is supplied externally from connector J8 as shown in 図 6. Each of the bottom LMG3410 has a 2.2- $\mu$ F decoupling capacitor (C95 in 図 5). 図 3 calculates the current requirement for the gate drive power supply. The current consumption is considered maximum worst case from their respective datasheets. The 6.5 mA for the ISO7831 is the current consumed on the high-voltage side bias at 5 V and for a square waveform with a 1-Mb bandwidth.

表 3. Current Consumption of Gate Drive Power Supply

CIRCUIT POWERED FROM GATE DRIVE POWER SUPPLY	CURRENT
6 x LMG3410 (100 kHz)	6 x 6mA
6 x ISO7831 high side	6 x 6.5mA
3 x AMC1306 high side	4 x 3.6mA
Total	89.4 mA

 

Copyright © 2017, Texas Instruments Incorporated

図 6. Power Supply Input of Gate Drive Schematic

### 2.3.1.5 Bootstrap Power Supply

The top three LMG3410 is powered by a bootstrap power supply configuration consisting of a bootstrap capacitor ( $C_{BOOT}$  is C80 in [Figure 5](#)), bootstrap diode (D5 in [Figure 5](#)) and bootstrap resistor ( $R_{BOOT}$  is R48 in [Figure 5](#)). This method has the advantage of being simple. The maximum voltage that the bootstrap capacitor ( $V_{BS}$ ) can reach is dependent on the elements of the bootstrap circuit. Consider the voltage drop across  $R_{BOOT}$ ,  $V_F$  of the bootstrap diode, and the drop across the low-side switch ( $V_{DS\_ON}$ , depending on the direction of current flow through the switch). Also, before the inverter is started, the bottom GaN module should be turned on for a sufficient duration to allow the bootstrap capacitor to charge.

### 2.3.1.6 Selection of Bootstrap Capacitor ( $C_{BOOT}$ )

The bootstrap capacitor is charged when the bottom GaN module is on and is discharged when the top GaN module is on.  $C_{BOOT}$  must be sized to maintain enough voltage throughout the PWM period. The current required to supplied is 6 mA (LMG3410 at a 100-kHz PWM) + 3.6 mA (ISO7831) + 6.5 mA (AMC1306) = 16.1 mA. For 100 kHz, the PWM period is 10  $\mu$ s. This corresponding charge that has to be stored on  $C_{BOOT}$  is 10  $\mu$ s  $\times$  16.1 mA = 0.161  $\mu$ C. Good guideline is to size  $C_{BOOT}$  to store ten times the charge over the PWM period (that is,  $C_{BOOT}$  should store  $Q_{BOOT} = 10 \times 0.161 \mu$ C). The bootstrap capacitor has to supply this charge.  $C_{BOOT}$  is calculate as  $Q_{BOOT} / \Delta V_{BOOT}$ , which is 1.7  $\mu$ C/1V = 1.7  $\mu$ F.  $C_{BOOT}$  is chosen to be 2.2  $\mu$ F.

### 2.3.1.7 Selection of Bootstrap Diode

The voltage that the bootstrap diode encounters is the same as the full DC bus voltage (in this case, a maximum of 600-V DC). The bootstrap diode voltage rating must be greater than the DC bus rail voltage. The bootstrap diode must be a fast recovery diode to minimize the recovery charge and thereby the charge that feeds from the bootstrap capacitor from the 15-V supply. The diode must be able to carry a pulsed peak current of 4.43 A (discussed in [2.3.1.8](#)). However, the average current is much smaller and depends on the switching frequency and the bootstrap charge. The selected diode is UFM15PL which is a 600-V, 1-A diode with a fast reverse recovery.

The bootstrap diode power dissipation ( $P_{D_{BOOT}}$ ) can be estimated based on the switching frequency, diode forward voltage drop, and the switching frequency of the PWM signal ( $f_{SW}$ ). In this TI Design, the switching frequency has been set to 100 kHz. The estimated power loss for the bootstrap diode is

$$P_{D_{BOOT}} = \frac{1}{2} \times Q_{BOOT} \times V_{D_{BOOT}} \times f_{SW} = 0.5 \times 1.7 \mu\text{C} \times 1.7 \text{ V} \times 100 \text{ kHz} = 144.5 \text{ mW}.$$

### 2.3.1.8 Selection of Current Limiting Resistor for Bootstrap Diode ( $R_{BOOT}$ )

The bootstrap charge  $Q_{BOOT}$  flows through  $R_{BOOT}$  for a charging time of 0.3  $\mu$ s; the average resistor current should be  $I_{CH} = Q_{BOOT} / t = 0.161 \mu\text{C} / 0.3 \mu\text{s} = 0.53 \text{ A}$ .

With the voltage drop across the diode being 1.7 V,  $R_{BOOT} = V_{D_{BOOT}} / I_{CH} = 1.7 \text{ V} / 0.53 \text{ A} = 3.2 \Omega$ .

This TI Design uses an  $R_{BOOT}$  value of 3  $\Omega$ .

The peak resistor current is  $(15 \text{ V} - V_{D_{BOOT}}) / R_{BOOT} = (15 \text{ V} - 1.7 \text{ V}) / 3 \Omega = 4.43 \text{ A}$ . The  $R_{BOOT}$  resistor should be able to supply this peak current and the average current of 0.53 A.

### 2.3.1.9 Thermal Design

The aim of the thermal design is to ensure the TIDA-00915 board can deliver the rated power without exceeding the maximum junction temperature of the GaN modules. The temperature depends on power loss occurring inside the GaN module, the power loss is also the heat generated on the board. Considering an efficiency of 98% at the rated power of 1.5 kW, the corresponding power loss on the board is 30.6 W. This power loss is distributed across each GaN module, hence the power loss per GaN module is  $(30.6 \text{ W}) / 6 = 5.1 \text{ W}$ .

The LMG3410 datasheet gives the thermal specification of  $\theta_{JA}$  while operating in still air of  $26.5^\circ\text{C/W}$ . When operating at 5.1 W, the temperature rise of the LMG3410 junction is  $5.1 \text{ W} \times 26.5^\circ\text{C/W} = 135^\circ\text{C}$ . This value is more than the  $125^\circ\text{C}$  rating of the LMG3410.

A heat sink with fan cooling is chosen. The fan is assumed to give 800 LFM of air flow to operate the heat sink at max thermal efficiency. Approximate thermal calculations with heat sink shown in 表 4 with assumption of equal distribution of the power loss between the six GaN modules.


表 4. Thermal Impedance Estimation of Three-Phase GaN Inverter

COMPONENT	THERMAL IMPEDANCE ( $\theta$ )	THERMAL IMPEDANCE ( $\theta$ ) FOR 6 GaN MODULES
LMG3410 GaN module $\theta_{JC}$	$0.5^\circ\text{C/W}$	$= 0.5 / 6 = 0.084^\circ\text{C/W}$
24 thermal via (10-mil diameter and 17.5- $\mu\text{m}$ via copper thickness)	$11.375^\circ\text{C/W}$	$= 11.375 / 6 = 1.895^\circ\text{C/W}$
Thermal interface material (Part number: Tgard™ K52-1)	$0.9^\circ\text{C-cm}^2 / \text{Watt}$ / (Copper plane area under LMG3410) $= 0.9^\circ\text{C-cm}^2 / \text{Watt}$ / $(0.45 \text{ cm} \times 0.8 \text{ cm}) = 0.324^\circ\text{C/W}$	$= 0.324 / 6 = 0.054^\circ\text{C/W}$
Extrusion heat sink with 800 LFM (Part number: ATS-EXL65-300-R0)	$= (2.4 \text{ C/W per inch}) / \text{Extrusion length} = 2.4 / 5.9 = 0.407^\circ\text{C/W}$	$= 0.407^\circ\text{C/W}$

At 32 W, the temperature rise is  $2.44^\circ\text{C/W} \times 30.1 = 73.44^\circ\text{C}$ . The estimated room temperature of a  $23^\circ\text{C}$  junction temperature would be  $73.44^\circ\text{C} + 23^\circ\text{C} = 96.44^\circ\text{C}$ . There is a head room of  $28^\circ\text{C}$ , which limits the maximum ambient to  $50^\circ\text{C}$ .
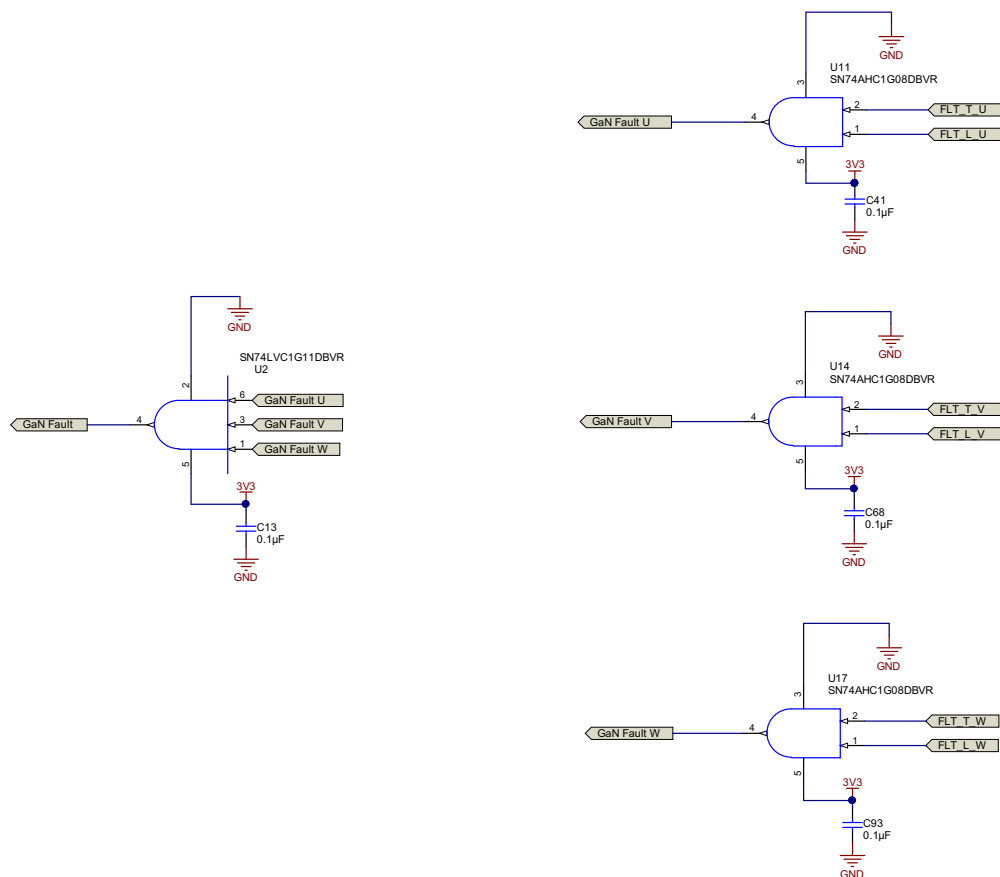
### 2.3.1.10 Inverter Protection and $\overline{\text{FAULT}}$ Feedback

The LMG3410 has UVLO, overcurrent detection, and overtemperature with latched turnoff of the GaN FET. The UVLO is used to prevent improper operation due to a failing gate drive power supply. The overtemperature and overcurrent protection ensure the GaN FETs are protected against short circuit faults of the inverter. There are six GaN modules each with a  $\overline{\text{FAULT}}$  signal, which are brought to the low-voltage side using digital isolators. The fault signals are combined using the logic circuit shown in 図 7.




Copyright © 2017, Texas Instruments Incorporated

図 7. Logic Circuit to Group FAULT Signals Schematic
 
### 2.3.2 5- and 3.3-V Low-Voltage Power Rail

An external 5-V power supply is required to bias all the circuits on the low-voltage side of the board. 図 8 shows the 5-V rail input. The diode D2 protects against accidental reverse biasing the 5-V rail. The TLV1117-3 is the LDO used for generating the 3.3-V rail.



Copyright © 2017, Texas Instruments Incorporated

図 8. 3.3-V Power Supply LDO Schematic

表 5 shows the power consumption by the different circuit biased by the 3.3-V rail. There are three AMC1306 devices, six digital isolators, an indication LED, and FAULT grouping using AND gates powered from this 3.3-V rail. The current consumption is considered maximum worst case from their respective datasheets. The 4 mA for ISO7831 is the current consumed on the low-voltage side bias at 3.3 V and for a square waveform with a 1-Mb bandwidth.


表 5. Current Consumption of 5-V Rail Power Supply

CIRCUITS POWERED FROM 3.3-V LDO	CURRENT
ISO7831 × 6	6 × 4 mA
AMC1306 × 4	4 × 3.6 mA
Clock termination resistors ×1	1.65 mA
SN74AHC1G08 × 3	3 × 4 mA
SN74LVC1G11 × 1	16 mA
Indication LED × 1	10 mA

The total worst case power consumption is about 78 mA. The power dissipation in the LDO is  $P = (V_{IN} - V_{OUT}) \times I_{OUT} = (5 - 3.3) \times 0.078 = 0.1326 \text{ W}$ .
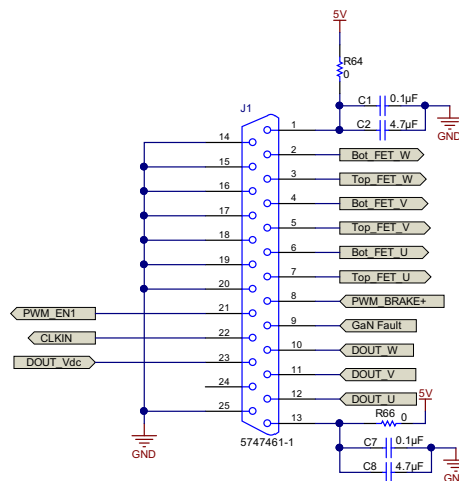
### 2.3.3 Signal Interface to Controller

A DB-25 connector is used for the signal interface connector. 図 9 shows the different signal between interfaced to the inverter on the signal interface connector. The 5 V is given from power stage to the TIDA-00915-Controller to power the C2000 control card through the signal interface connector. This routing of the 5-V power rail is done to have the 5-V rail in a star network with the center on the TIDA-00915 board. The 5 V is required to be supplied to the TIDA-00915-Controller, where the 5-V rail is stepped down to 3.3 V by an LDO to power the C2000 MCU on the control card. The interface signals are all 3.3-V logic signals. The multiple ground lines are used on the connector to ensure a solid ground connection to prevent ground bounce issues.



Copyright © 2017, Texas Instruments Incorporated


図 9. Signal Interface Connector to Controller Schematic

## 2.3.4 TIDA-00915 Controller


The TIDA-00915-Controller is adapter board between the 180-pin C2000 F28379D control card and the TIDA-00915 GaN inverter. The TIDA-00915-Controller has the same DB-15 signal interface connector as the TIDA-00915 GaN inverter. The inverter and the controller are connected using a DB-15 ribbon cable.

Figure 10 shows the important parts of the board used for testing. There are additional features on the TIDA-00915-Controller that are not used in this TI Design.


Connection to Delfino Control Card

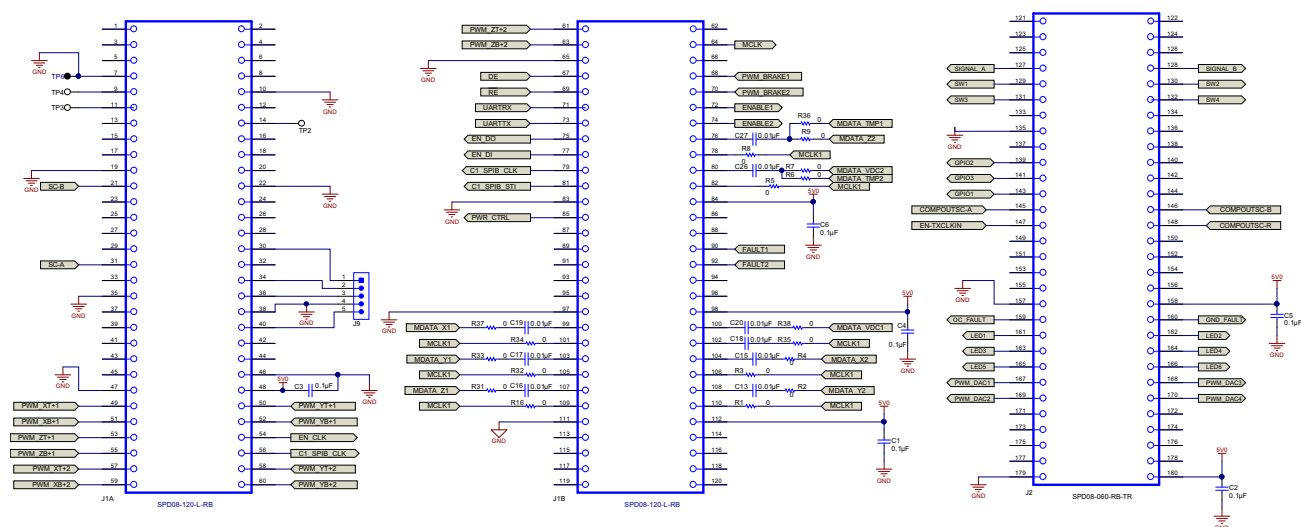

Clock Buffer

 

Signal Interface Connector to Inverter

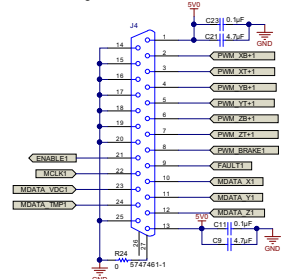

Copyright © 2017, Texas Instruments Incorporated

Figure 10. TIDA-00915 Controller Schematic



### 3 Getting Started Hardware and Software

#### 3.1 Hardware

 


図 11. TIDA-00915 PCB and TIDA-00915-Controller Top Side

 


図 12. TIDA-00915 PCB Bottom Side

 


図 13. Heat Sink With Electrically Insulated Thermal Interface Material

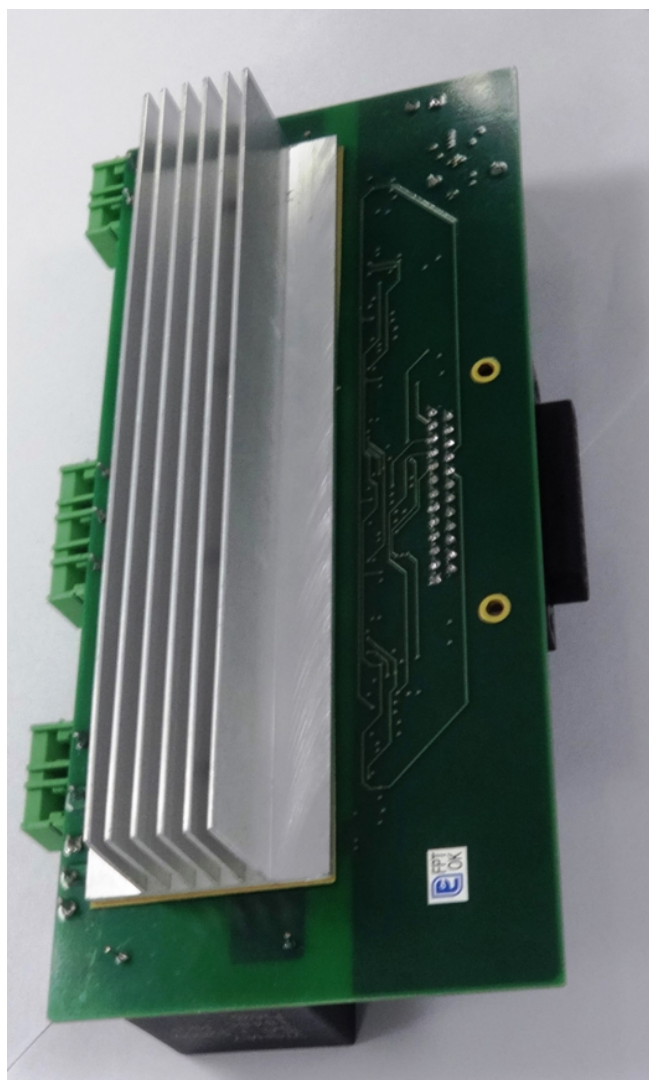


図 14. Heat Sink Mounted on Bottom Side of TIDA-00915 PCB

図 15 shows the fan used for cooling. There is an encasing around the fan to duct the airflow from top to under the PCB where the heat sink is located. 図 16 shows the position of the fan with respect to the heat sink.

 


図 15. Fan With Duct

 


図 16. Position of Air Flow and Heat Sink



**表 6. Signal Interface Connector Pin Description on TIDA-00915**

PIN NUMBER	PIN NAME	I/O	DESCRIPTION
1	5V	Power	5-V power to TIDA-00915-Controller
2	Bot_FET_W	3.3-V input	Phase W lo-side gate driver PWM input
3	Top_FET_W	3.3-V input	Phase W hi-side gate driver PWM input
4	Bot_Fet_V	3.3-V input	Phase V lo-side gate driver PWM input
5	Top_FET_V	3.3-V input	Phase V hi-side gate driver PWM input
6	Bot_FET_U	3.3-V input	Phase U lo-side gate driver PWM input
7	Top_FET_U	3.3-V input	Phase U hi-side gate driver PWM input
8	PWM_BRAKE+	3.3-V input	PWM input to brake IGBT gate driver
9	GaN Fault	3.3-V output	FAULT signal combined from all LMG3410 modules
10	DOUT_W	3.3-V output	Phase W current measurement data from delta-sigma modulator
11	DOUT_V	3.3-V output	Phase V current measurement data from delta-sigma modulator
12	DOUT_U	3.3-V output	Phase U current measurement data from delta-sigma modulator
13	5V	Power	5-V power to TIDA-00915-Controller
14	GND	Power	Low-voltage side ground
15	GND	Power	Low-voltage side ground
16	GND	Power	Low-voltage side ground
17	GND	Power	Low-voltage side ground
18	GND	Power	Low-voltage side ground
19	GND	Power	Low-voltage side ground
20	GND	Power	Low-voltage side ground
21	PWM_EN1	3.3-V input	Enable receiving GaN Fault Signal
22	CLKIN	3.3-V output	Clock input to TIDA-00915 from the control card
23	DOUT_Vdc	3.3-V output	DC bus voltage measurement data from delta sigma modulator
24	NC	NA	NA
25	GND	Power	Low-voltage side ground



## 4 Testing and Results

表 7 lists the key test equipment. The board is powered from three power supplies: 300 V for the DC-link, 15 V for the gate drive power supply, and 5 V for the low-voltage side bias. All power supplies are isolated from each other.

The following subsections provide descriptions and pictures of the test setup for each specific test.

表 7. Key Test Equipment

DESCRIPTION	PARTNUMBER
High-speed oscilloscope	Tektronix MSO2024B
Isolated oscilloscope	Tektronix TPS2014B
High-voltage probes	Keysight 10076B
Low-voltage probes	Tektronix TPP0200
Isolated current probe	Keysight N2781B
C2000 F28379D control card	Texas Instruments TMDSCNCD28379D
Adjustable power supply	Keithley 2230G-30-1
High-voltage power supply	Sorensen SGI 1000/5
Thermal camera	Fluke Ti400
Power analyzer	Tektronix PA4000
Inverter load	3.7 kW, 1460 rpm (0.5 to 100 Hz), 415 V <sub>RMS</sub> ± 10%, $\eta$ = 83 %, $\cos\phi$ = 0.74, 8.4 A <sub>MAX</sub>

### 4.1 Bootstrap Power Supply Ripple

The bootstrap voltage across the bootstrap capacitor is monitored to verify that the rail has charged up to the expected gate drive voltage and is able to maintain the voltage throughout the entire switching cycle. This test is done with the inverter DC-link at 300 V and supplying a no-load current to the motor. The switching frequency is set at 48 kHz.

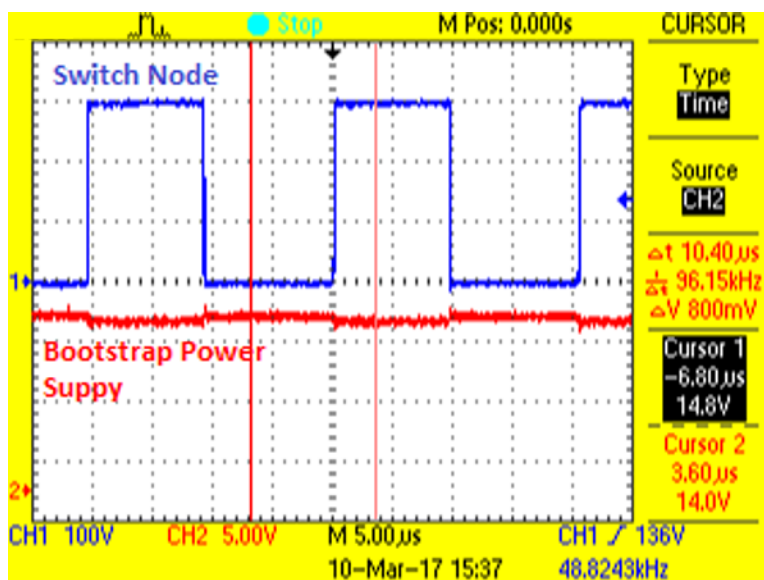


図 18. Switch Node Voltage and Bootstrap Power Supply

Figure 18 shows the bootstrap power supply charges to 14.8 V when the switch node voltage is low this is when the bottom GaN module is on and the top is off. The voltage drops to 14 V when the switch node voltage is high; this is when the bottom GaN module is off and the top is on. The drop is because the bootstrap cap is floating and the capacitor discharges when the top GaN module turns on. The total power supply ripple is 0.8 V.

## 4.2 Invert Output $dV/dt$ and Ringing

An inverter is required to operate up to a maximum  $dV/dt$  as permitted by the type of load connected and without excessive ringing across the FETs. The ringing can cause the FETs to fail if the ringing is above the absolute maximum voltage rating.

The switch node voltage is captured with a high-voltage probe with a bandwidth of 200 MHz. The inverter was running the motor without load. Figure 19 and Figure 20 show the rising edge of the u-phase switch node voltage, and Figure 21 and Figure 22 show the falling edge. This node is the furthest from the DC-link input terminal and more prone to ringing due to a larger power trace inductance. The oscilloscope is set up to trigger when the edge transition time is less than the trigger threshold time. This corresponds to the highest  $dV/dt$ , which is also when the half bridge is hard switching.

 


Figure 19. Rising Edge Switch Node Waveform

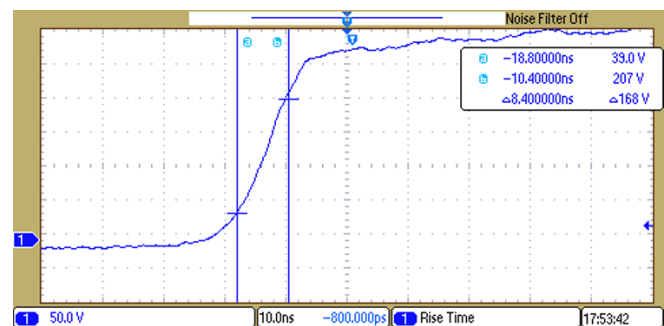


Figure 20. Rising Edge Switch Node Waveform Zoomed

 


Figure 21. Falling Edge Switch Node Waveform

 


Figure 22. Falling Edge Switch Node Waveform Zoomed

Figure 19 and Figure 21 show that there is no visible ringing at the end of rising edge or the falling edge of the switch node. The ringing happens in silicon FETs as it is oscillation between FET output capacitance the parasitic trace inductance. The ringing in a GaN-based inverter is absent as the GaN FET has very small output capacitance. The rising and falling  $dV/dt$  is measure to be 20 V/ns and 21 V/ns, respectively.



### 4.3 Inverter Power Losses

The inverter power loss is obtained using a power analyzer, which measures the input power at the DC-link terminal and the output power at the three phase inverter output terminal. The difference between input and output power is the power loss. This test is done at 300 V and the inverter is loaded by the motor. 図 24 is the power loss versus the output line current of the inverter.

 


図 23. Test Setup for Inverter Power Loss

 


図 24. Inverter Power Loss

Inverter efficiency is derived from the power loss by calculating the output power and input power. The output power is obtained from 式 1 where:

- $V$  is the maximum RMS voltage from the inverter, calculated as DC-Link Voltage  $\times 1.15 / \sqrt{2}$ .
- $I_{\text{RMS}}$  is the line current used in 図 24 for the inverter power loss
- PF is the power factor for a permanent magnet servo motor the power factor is near 1.

The input power is obtained from  $P_{\text{IN}} = P_{\text{OUT}} + P_{\text{LOSS}}$ .

Efficiency  $\eta = P_{\text{OUT}} / P_{\text{IN}} \times 100$ .

図 25 is the inverter efficiency plotted versus the output power and also the inverter current.

 


図 25. Inverter Efficiency versus Inverter Current Output Power

#### 4.4 Thermal Characteristics

This test verifies the safe operation of the inverter with the chosen heat sink and fan cooling with the PCB in an open environment. However, characteristics depend on the amount of cooling available, hence results can vary in the end product depending on if more or less cooling available. This test should be only taken for guidance that a small thermal solution is possible for a 2-kW inverter and is made possible by the low-power loss of the GaN module-based inverter.

 


図 26. Heat Sink Temperature versus Inverter Output Current

 


図 27. Inverter Thermal Image at 24-kHz and 4.5-A<sub>RMS</sub> Inverter Output Current


 


図 28. Inverter Thermal Image at 100-kHz and 4.5-A<sub>RMS</sub> Inverter Output Current

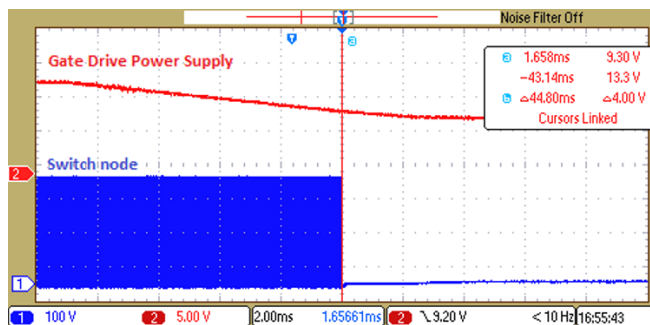
## 4.5 Undervoltage Protection for Inverter Gate Drive Power Supply

Under normal operation, the inverter is started after all the power rails have reached their proper voltage level. There may be a condition that the power supply of the gate drive has failed and the voltage is below the recommended value. This situation is prevented by the detection of undervoltage and disabling the turnon of the gate driver inside the LMG3410 GaN module.


The UVLO is verified by powering the DC-link from a 300-V power supply and the inverter is given a PWM of 100 kHz with a constant duty. The bench power supply connected to the gate drive power supply is turned off. The point at which the switch node stops giving a PWM is when the UVLO is activated when the voltage is falling. Similarly, the power supply of the gate drive is turned on and the point at which the switch node start gives a PWM is where the UVLO is deactivated.



 
☒ 29. UVLO Activation due to Falling Gate Drive Power Supply



 ☒ 30. Zoomed in UVLO Activation due to Falling Gate Drive Power Supply



 ☒ 31. UVLO Deactivation due to Rising Gate Drive Power Supply



☒ 32. Zoomed in UVLO Deactivation due to Rising Gate Drive Power Supply

☒ 30 shows the UVLO is activated at 9.1 V and ☒ 32 UVLO is deactivated at 10.1 V. There is a hysteresis of 0.5 V between the activation and deactivation of the UVLO.

## 4.6 Inverter Overcurrent Protection

This test validates effectiveness of the overcurrent trip provided inside the LMG3410 to protect the three-phase inverter.

For the test an overcurrent situation is created in the inverter when driving an induction motor. The motor is suddenly over magnetized by suddenly reducing the frequency of the space vector PWM while the voltage vector is kept constant.

Figure 33 shows the result of the test, where the waveforms are triggered when **FAULT** signal is activated along with one of the inverter line current. The **FAULT** signal is the grouped fault signal (**GaN\_FAULT**) from all the LMG3410 modules in the inverter. The PWM frequency is 100 kHz.

 


図 33. Overcurrent Fault Detection

The current triggering the **FAULT** signal low is about 24.8 A. The line current reduces to zero as the GaN FET carrying this current has been turned off internally. The PWM controller may use the **FAULT** feedback to turn off the remaining PWM.

注: All GaN FETs are protected from overcurrent at any time, and when overcurrent is detected, the turnoff is latched. The latched turnoff can only be removed if PWM signal is held low for 350 µs.

## 5 Design Files

### 5.1 Schematics

To download the schematics, see the design files at [TIDA-00915](#).

### 5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-00915](#).



## 5.3 PCB Layout Recommendations

 


図 34. Layout Recommendation

### 5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-00915](#).

### 5.4 Altium Project

To download the Altium project files, see the design files at [TIDA-00915](#).



## 5.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-00915](#).

## 5.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-00915](#).

## 6 Software Files

To download the software files, see the design files at [TIDA-00915](#).

## 7 Related Documentation

1. Texas Instruments, [High Voltage Half Bridge Design Guide for LMG3410 Smart GaN FET](#), Application Report (SNOA946)
2. Texas Instruments, [GaN FET module performance advantage over silicon](#), White Paper (SLYY071)

### 7.1 商標

C2000, controlSUITE are trademarks of Texas Instruments.  
Tgard is a trademark of Laird Technologies, Inc.

## 8 Terminology

**GaN**— Gallium nitride

**IGBT**— Isolated gate bipolar transistor

**UVLO**— Undervoltage lockout

**CMTI**— Common-mode transient immunity

**HEMT**— High electron mobility transistor

## 9 About the Authors

**NELSON ALEXANDER** is a systems engineer at Texas Instruments where he is responsible for developing reference design solutions for the industrial drives.

**N. NAVANEETH KUMAR** is a system architect in the Industrial Systems-Motor Drive team at Texas Instruments, where he is responsible for specifying and developing reference designs for industrial drives.

## TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関係する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに同意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任がお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的での、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または黙示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジーまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものでもありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、あるいはTIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的にかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、続発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する黙示の保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁済または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際の、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知らされていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかったために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/sampterms.htm>)についてのTIの標準条項が含まれますが、これらに限られません。